

Fig: CKT diagram of transformer coupled Amplifier

→ The input Impedance of an amplifier is low while its output impedance is very high.
→ When they are coupled to make a multi stage amplifier, the high output impedance of one stage come in parallel with the low input impedance of the next stage. Hence, effective load (R_{eq}) is decreased.

→ The resistance on the secondary side of a transformer reflected on the primary depend upon the turn ratio of the transformer.

* Operation of Principle

→ When an a.c. signal is applied to the base of first transistor it appears in the amplified form across primary "p" of the coupling transformer to the input of the next stage by the secondary transformer.
→ The next stage renders amplification in an exact similar manner. Amplification in the an exactly similarly manner.


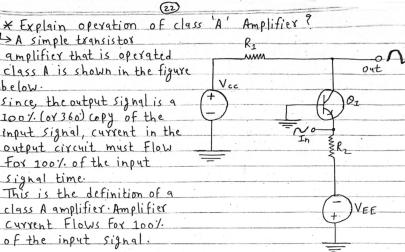


Fig: A simple class A transistor amplifies

→ The class A amplifier has the characteristics of good fidelity and low efficiency. Fidelity means that the output signal is just like the input signal in all respects except amplitude. It has the same shape and frequency.
→ In some cases, there may be a phase difference between input and output signal (usually 180°) but the signals are still considered to be "good copies".

* Class "C" amplifier.

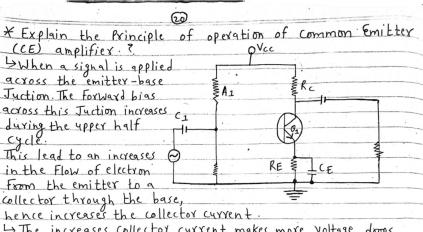→ The output signal most bears very little resemblance to the input signal. Class "C" amplifiers are used where the output signal need only be present during parts of one-half of the input signal. Any amplifier that operates on less than 50% of the input signal is operated class "C".



→ Explain the principle of operation of common emitter (CE) amplifier?
→ When a signal is applied across the emitter-base junction, the forward bias across this junction increases during the upper half cycle. This leads to an increase in the flow of electrons from the emitter to the collector through the base, hence increasing the collector current.
→ The increased collector current makes more voltage drops across the collector load resistance RC.
→ The negative half cycle decreases the forward bias voltage across the emitter-base junction.
→ This decreases the collector base voltage, decreases the collector base current in the hole collector resistance RC.
→ Thus, the amplifier load resistor appears across the collector resistor. The common emitter circuit is shown above.

* Characteristics of common emitter amplifier.

→ The voltage gain of common emitter amplifier is medium and also current gain is medium.
→ The power gain of common emitter circuit is high.
→ Input/output is having a phase relation of 180°.
→ Input and output resistance of common emitter amplifier is medium.

CS CamScanner

* What is Multiplexer (MUX)? Explain operation of 4x1 multiplexer. With circuit diagram and truth table.
→ A multiplexer (MUX) is a network device that allows one or more analog or digital input signals to travel together over the same communications transmission link.
→ It has many input lines and only one output line. It is also known as data selector.
→ The inputs are selected by selection line. e.g. 4x1 MUX, 8x1 MUX, 16x1 MUX
→ A multiplexer is a combinational circuit that has 2ⁿ input lines and a single output line.

* 4x1 Multiplexer (MUX)

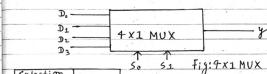


Fig: 4x1 MUX

Selection line	Output	
S ₀	S ₁	Y
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

Fig: Truth table.

$$Y = D_0 \bar{S}_0 \bar{S}_1 + D_1 \bar{S}_0 S_1 + D_2 S_0 \bar{S}_1 + D_3 S_0 S_1$$

→ A 4x1 MUX consists of four data input lines (D₀ to D₃), two select lines (S₀ and S₁) and a single output line (Y). The select lines S₀ and S₁ select one of the four input lines to connect the output line.

CS CamScanner

* Define Flip-flop? Explain the operation of 'D' flip-flop with suitable diagram & truth table.

→ A flip-flop in digital electronics is a circuit with two stable states that can be used to store binary data.
→ The stored data can be changed by applying varying inputs.

* D-Flip-flop or Delay or Data Flip-flop

→ It is also known as delay flip-flop.
→ It has only one data input that is 'D' and one clock pulse input CK. With two outputs S and Q. This flip-flop is also called a delay flip-flop. Fig: Block Diagram. because when the input data is provided into the D flip-flop, the output follows the input.

Data delay by one clock pulse
→ The given circuit represents the D flip-flop CKT diagram. Where the whole circuit is designed with the help of the NAND gate. Here the output of one NAND gate is feed as one input to the other NAND gate, which forms a latch. Then the latch is gated with two more NAND gate where D is one input and clock is the other input.

Q(t)	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

Fig: Truth table.

S _{t+1}	Q _t	Q _{t+1}
0	0	1
1	0	0

Fig: Characteristics table.

CS CamScanner

* Explain photo diode and its operation characteristics?

An: Photo diode:

→ A photo diode is a reverse-biased silicon or Germanium P-N Junction in which reverse current increases when the junction is exposed to light.

→ When no light is incident on the PN-Junction, the reverse current I_R is extremely small.

→ The resistance of photo diode with no incident light is called dark resistance.

$$(RR) : i.e. RR = VR / IR$$

An: Characteristics.

① Reverse Voltage-Reverse Current curve:
→ Show the graph between reverse current (I_R) and reverse voltage (VR) for various illumination levels.


→ It is clearly reverse-biased voltage (VR) and reverse current (I_R) increases as the illumination (E) on the P-N Junction.

→ Opto Coupler (or optoisolator):

→ An opto couple is also called optoisolator is a device that uses light to couple a signal from its input (photo emitter, e.g. LED) to its output (photo detector, e.g. photo diode).

→ The working principle is an interesting a power full light emitting diode (LED) is connected across a variable sources.

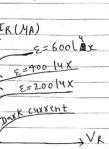→ A current is first applied to the opto couple, which makes the infrared LED emit a light that's proportional to the current.



* Digital to analog conversion?

→ Digital to analog conversion (DAC) is the process of converting a digital signal to an analog signal. This is typically done by assigning a voltage or current value to each discrete digital value and then using these values and then using these values to reconstruct a continuous analog wave form.

→ The resulting analog signal can then be used to drive various types of analog output devices such as speakers, motors or control systems.

→ DACs can be found in a wide range of electronic devices including audio systems, video displays and sensors to convert digital data streams into analog audio signals.

Digital Input $\xrightarrow{\text{DAC}}$ Analog output
Fig: DAC symbol.

* Analog to digital conversion (ADC)?

→ Analog to digital conversion (ADC or A/D) is the process of converting a continuous analog signal into a discrete digital representation.

→ This is typically done by sampling the analog signal at regular intervals and measuring its amplitude at each sample point.

→ The resulting sequence of digital values can then be stored processed or transmitted digitally.

→ The quality of the digital representation is determined by factors such as the resolution of the converter, the sampling rate and the accuracy of the measurement circuitry.

→ ADC is widely used in various applications such as audio recording, instrumentation, and control systems.

Input analog $\xrightarrow{\text{ADC}}$ digital output.

CS CamScanner